

N (Printed Pages 4)

(20517) Roll No.....

B.C.A. - II Sem.

18007

B.C.A. Examination, May 2017

Digital Electronics and Computer

Organisation

(BCA-204)

(New)

Time : Three Hours] Maximum Marks : 75

Note : Attempt all the sections as per instructions.

Section-A

Note : Attempt all five questions. Each question carries three marks.

- 1. What is truth table? What is its significance? 3
- 2. What is multiplexers? 3

P.T.O.

- 3. Explain the Edge Triggered D Flip-Flops. 3
- 4. Why are NAND and NOR gates more popular? 3
- 5. Difference between Registers and Counters. 3

Section-B

Note : Attempt any two questions.

- 6. Reduce the following Boolean expression using K-Map. 7.5
 $F(P, Q, R, S) = \Sigma(0, 3, 5, 6, 7, 11, 12, 15)$
- 7. The 2732 is a 4096 x 8 EPROM. How many address line does it have? 7.5
- 8. Draw the master slave JK flip-flop and explain its working. 7.5

1800712

Section-C

Note : Attempt any **three** questions.

9. (a) Explain the difference between cache memory and virtual memory. 7.5
- (b) Draw the Half adder Logic circuit and summarize the operation. 7.5
10. (a) State and verify De Morgan's Law in following Boolean Algebra. 7.5
- (b) Draw a Logic Circuit Diagram for the Boolean expression 7.5
- $$X : (Y'+Z)$$
11. (a) Explain the operation of the bi-directional shift register. 7.5
- (b) Explain how a J-K flip-flop can be converted into a D flip-flop. 7.5

1800713

P.T.O.

12. Define the following : 3×5=15
- (a) Multiplexer (8×1) MUX Design
- (b) Register
- (c) Flip-Flop Application
- (d) Asynchronous Counter
- (e) Basic Cell of Static RAM
13. Write short notes on cache memory organization. 15

1800714